

Spiral 1 / Unit 2

Basic Boolean Algebra

Logic Functions

Decoders

Multiplexers

© Mark Redekopp

Outcomes

- I know the difference between combinational and sequential logic and can name examples of each.
- I understand latency, throughput, and at least 1 technique to improve throughput
- I can identify when I need state vs. a purely combinational function
 - I can convert a simple word problem to a logic function (TT or canonical form) or state diagram
- I can use Karnaugh maps to synthesize combinational functions with several outputs
- I understand how a register with an enable functions & is built
- I can design a working state machine given a state diagram
- I can implement small logic functions with complex CMOS gates

BOOLEAN ALGEBRA INTRO

Boolean Algebra

- A set of theorems to help us manipulate logical expressions/equations
- Axioms = Basis / assumptions used
- Theorems = manipulations that we can use


Axioms

- Axioms are the basis for Boolean Algebra
- Notice that these axioms are simply restating our definition of digital/binary logic
 - A1/A1' = Binary variables (only 2 values possible)
 - A2/A2' = NOT operation
 - A3,A4,A5 = AND operation
 - A3',A4',A5' = OR operation

(A1)	$X = 0 \text{ if } X \neq 1$	(A1')	$X = 1 \text{ if } X \neq 0$
(A2)	If $X = 0$, then $X' = 1$	(A2')	If $X = 1$, then $X' = 0$
(A3)	$0 \cdot 0 = 0$	(A3')	$1 + 1 = 1$
(A4)	$1 \cdot 1 = 1$	(A4')	$0 + 0 = 0$
(A5)	$1 \cdot 0 = 0 \cdot 1 = 0$	(A5')	$0 + 1 = 1 + 0 = 1$

Duality

 - Every truth statement can yields another truth statement
 - I exercise if I have *time and energy* (original statement)
 - I *don't exercise* if I *don't have time or don't have energy* (dual statement)
- To express the dual, swap...



Duality

- The “dual” of an expression is not equal to the original

$$\begin{array}{ccc} 1 + 0 & \neq & 0 \cdot 1 \\ \text{Original} & & \text{Dual} \\ \text{expression} & & \end{array}$$

- Taking the “dual” of both sides of an equation yields a new equation

$$\begin{array}{ccc} X + 1 = 1 & \Rightarrow & X \cdot 0 = 0 \\ \text{Original equation} & & \text{Dual} \end{array}$$

Single Variable Theorems

- Provide some simplifications for expressions containing:
 - a single variable
 - a single variable and a constant bit
- Each theorem has a dual (another true statement)
- Each theorem can be proved by writing a truth table for both sides (i.e. proving the theorem holds for all possible values of X)

T1	$X + 0 = X$	T1'	$X \cdot 1 = X$
T2	$X + 1 = 1$	T2'	$X \cdot 0 = 0$
T3	$X + X = X$	T3'	$X \cdot X = X$
T4	$(X')' = X$		
T5	$X + X' = 1$	T5'	$X \cdot X' = 0$

Single Variable Theorem (T1)

$$X + 0 = X \quad (T1)$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR

Hold Y constant

$$X \cdot 1 = X \quad (T1')$$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND

Whenever a variable is OR'ed with 0, the output will be the same as the variable...

"0 OR Anything equals that anything"

Whenever a variable is AND'ed with 1, the output will be the same as the variable...

"1 AND Anything equals that anything"

Single Variable Theorem (T2)

$$X + 1 = 1 \quad (T2)$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR

Hold Y constant

$$X \cdot 0 = 0 \quad (T2')$$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND

Whenever a variable is OR'ed with 1, the output will be 1...

"1 OR anything equals 1"

Whenever a variable is AND'ed with 0, the output will be 0...

"0 AND anything equals 0"

Single Variable Theorem (T3)

$$X + X = X \quad (T3)$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR

$$X \cdot X = X \quad (T3')$$

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND

Whenever a variable is OR'ed with itself, the result is just the value of the variable


Whenever a variable is AND'ed with itself, the result is just the value of the variable

This theorem can be used to reduce two identical terms into one OR to replicate one term into two.

Single Variable Theorem (T4)

$$(X')' = X \quad (T4)$$
 
$$\overline{\overline{X}} = X \quad (T4)$$



Anything inverted twice yields its original value

Single Variable Theorem (T5)

$$X + \bar{X} = 1 \text{ (T5)}$$

$$X \cdot \bar{X} = 0 \text{ (T5')}$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

AND


Whenever a variable is OR'ed with its complement, one value has to be 1 and thus the result is 1

Whenever a variable is AND'ed with its complement, one value has to be 0 and thus the result is 0

This theorem can be used to simplify variables into a constant or to expand a constant into a variable.


Application: Channel Selector

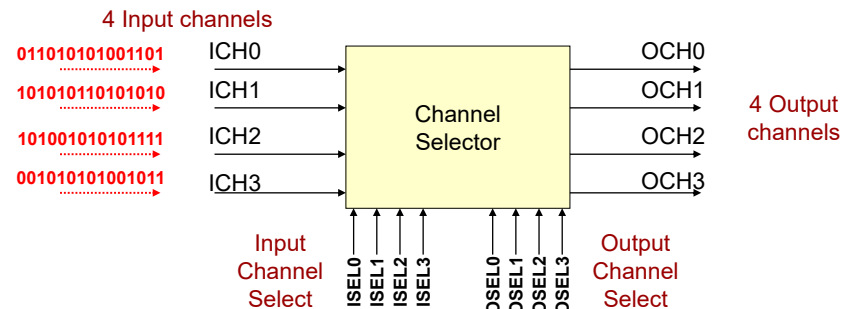- Given 4 input, digital music/sound channels and 4 output channels
- Given individual "select" inputs that select 1 input channel to be routed to 1 output channel




Application: Steering Logic

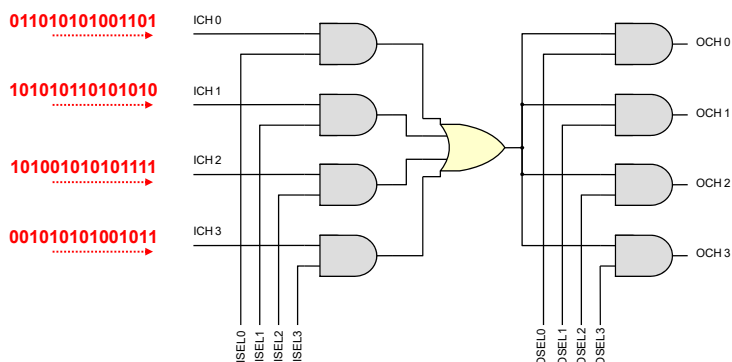- 4-input music channels (ICHx)
 - Select one input channel (use ISELx inputs)
 - Route to one output channel (use OSELx inputs)




Application: Steering Logic

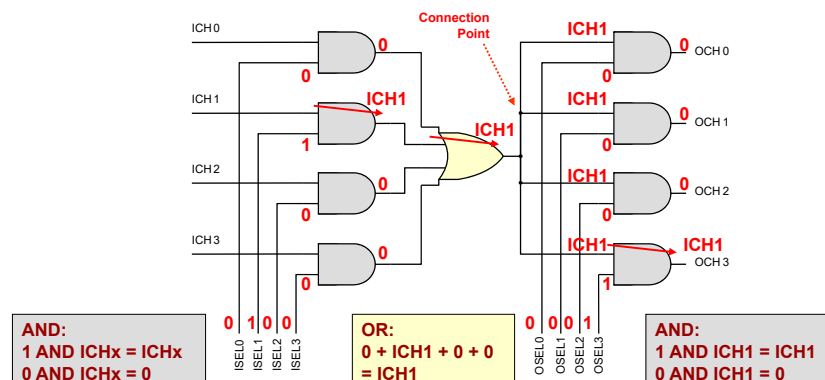- 1st Level of AND gates act as barriers only passing 1 channel
- OR gates combines 3 streams of 0's with the 1 channel that got passed (i.e. ICH1)
- 2nd Level of AND gates passes the channel to only the selected output



Your Turn


 
- Build a circuit that takes 3 inputs: S, IN0, IN1 and outputs a single bit Y.
- It's functions should be:
 - If S = 0, Y = IN0 (IN0 passes to Y)
 - If S = 1, Y = IN1 (IN1 passes to Y)



CHECKERS / DECODERS



Gates

  - Gates can have more than 2 inputs but the functions stay the same
 - AND = output = 1 if ALL inputs are 1
 - Outputs 1 for only 1 input combination
 - OR = output = 1 if ANY input is 1
 - Outputs 0 for only 1 input combination





Checkers / Decoders

  - An AND gate only outputs '1' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the AND gate as "checking" or "decoding" a specific combination and outputting a '1' when it matches.





Checkers / Decoders

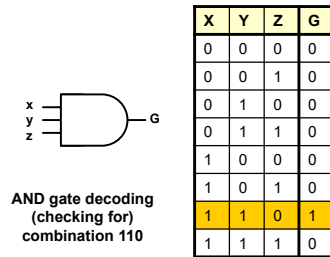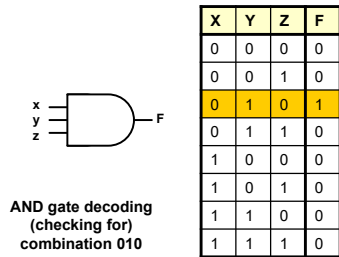- Place inverters at the input of the AND gates such that
 - F produces '1' only for input combination {x,y,z} = {010}
 - G produces '1' only for input combination {x,y,z} = {110}



Checkers / Decoders

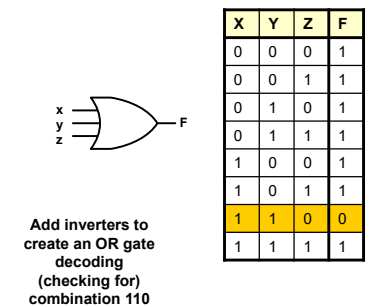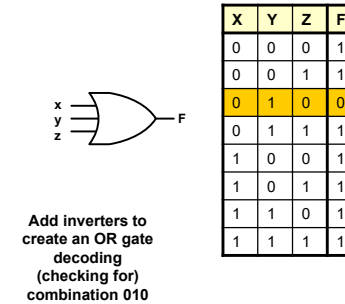- An OR gate only outputs '0' for 1 combination
 - That combination can be changed by adding inverters to the inputs



Decoder Exercise

- Design an instruction decoder that uses opcode[5:0] and func[5:0] as inputs and produces a separate output {ADD, SRL, SUB, etc.} for each instruction type that will produce '1' when that instruction is loaded

	opcode	rs	rt	rd	shamt	func
R-Type	000000	01000	10001	00101	00111	100000
	ADD	\$8	\$17	\$5	00000	
	000000	01000	10001	00101	00111	000010
	SRL	\$8	\$17	\$5	7	
	000000	01000	10001	00101	00111	100010
	SUB	\$8	\$17	\$5	7	
I-Type	opcode	rs	rt	immediate		
	001000	11000	00101	0000 0000 0000 0001		
	ADDI	\$24	\$5	20		
	100011	00011	00101	1111 1111 1111 1000		
	LW	\$3	\$5	-8		
	101011	00011	00101	1111 1111 1111 1000		
	SW	\$3	\$5	-8		
	000100	00011	00101	1111 1111 1111 1000		
BEQ	\$3	\$5	-8			
J-Type	opcode	Jump address				
	000010	Jump address				
	J	26-bits				


Decoder Exercise

	opcode	rs	rt	rd	shamt	func
R-Type	000000	01000	10001	00101	00111	100000
	ADD	\$8	\$17	\$5	00000	
	000000	01000	10001	00101	00111	000010
	SRL	\$8	\$17	\$5	7	
	000000	01000	10001	00101	00111	100010
	SUB	\$8	\$17	\$5	7	
I-Type	opcode	rs	rt	immediate		
	001000	11000	00101	0000 0000 0000 0001		
	ADDI	\$24	\$5	20		
	100011	00011	00101	1111 1111 1111 1000		
	LW	\$3	\$5	-8		
	101011	00011	00101	1111 1111 1111 1000		
	SW	\$3	\$5	-8		
	000100	00011	00101	1111 1111 1111 1000		
BEQ	\$3	\$5	-8			
J-Type	opcode	Jump address				
	000010	Jump address				
	J	26-bits				

Decoder Exercise

	opcode	rs	rt	rd	shamt	func
ADDI	000000	01000	10001	00101	00111	100000
	ADD	\$8	\$17	\$5	00000	
	000000	01000	10001	00101	00111	000010
LW	SRL	\$8	\$17	\$5	7	
	000000	01000	10001	00101	00111	100010
SW	SUB	\$8	\$17	\$5	7	
	opcode	rs	rt	immediate		
	001000	11000	00101	0000 0000 0000 0001		
	ADDI	\$24	\$5	20		
	100011	00011	00101	1111 1111 1111 1000		
	LW	\$3	\$5	-8		
	101011	00011	00101	1111 1111 1111 1000		
SW	SW	\$3	\$5	-8		
	000100	00011	00101	1111 1111 1111 1000		
	BEQ	\$3	\$5	-8		
J-Type	opcode	Jump address				
	000010	Jump address				
J		26-bits				


Single-Cycle CPU

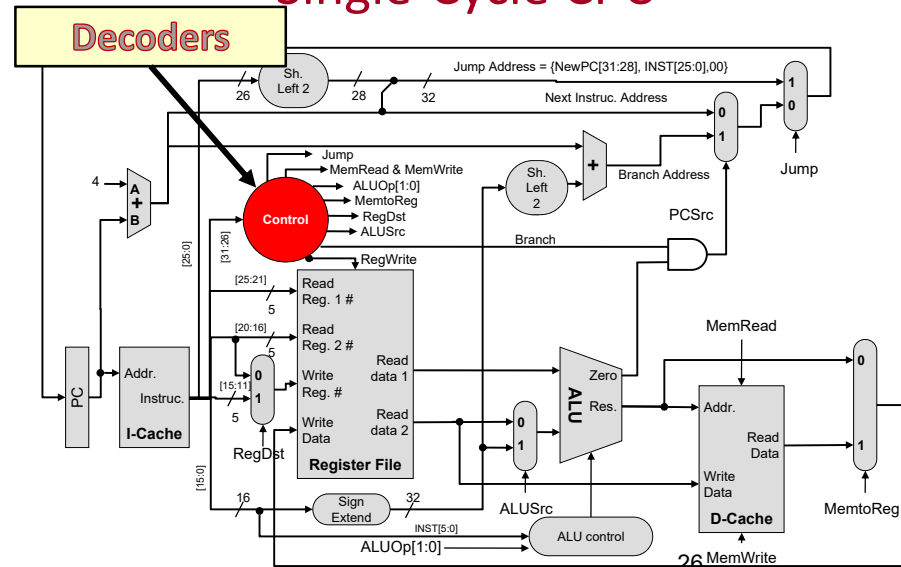

Full Decoders


- A full decoder is a building block that:
 - Takes in an n-bit binary number as input
 - Decodes that binary number and activates the corresponding output
 - Individual outputs for EVERY (MOST) input combination (i.e. 2^n outputs)

3-to-8 Decoder

 


Decoders

 - A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')




Decoders

 - A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')




Decoder Sizes

 - A decoder w/ an **n-bit input** has **2ⁿ outputs**
 - 1 output for every combination of the n-bit input




2-to-4 Decoder

 


3-to-8 Decoder

 Exercise

- Complete the design of a 2-to-4 decoder





Building Decoders


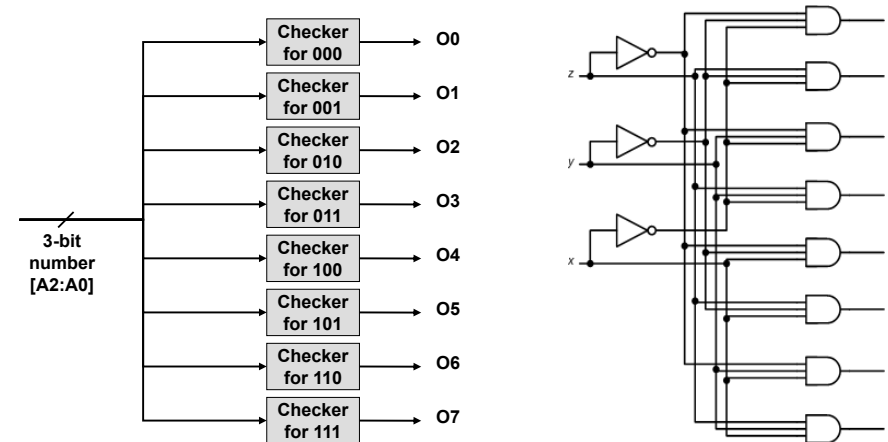


Enables

  - Exactly one output is active at all times
- It may be undesirable to always have an active output
- Add an extra input (called an enable) that can independently force all the outputs to their inactive values




Enables

  

Implementing Enables


- Original 2-to-4 decoder

 

When E=0, force all outputs = 0
When E=1, outputs operate as they did originally

Enables

 
- Enables can be implemented by connecting it to each AND gate of the decoder




When E=0, 0 AND anything = 0
When E=1, 1 AND anything = that anything, which was the normal decoding logic

Multiplexers

 
- Along with adders, multiplexers are most used building block
- n data inputs, $\log_2 n$ select bits, 1 output
- A multiplexer ("mux" for short) selects one data input and passes it to the output




Multiplexers

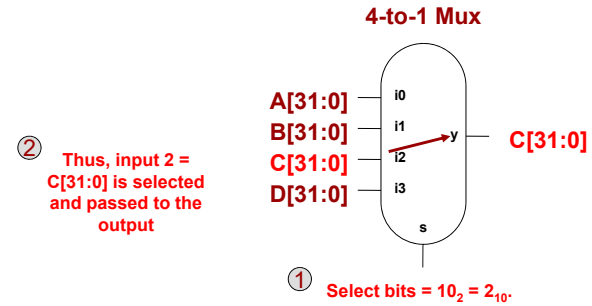

Multiplexers

 


Multiplexers

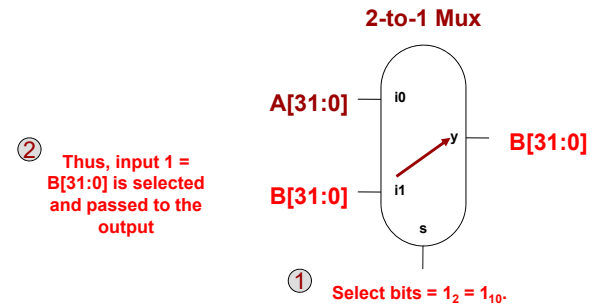


Recall Using T1/T2

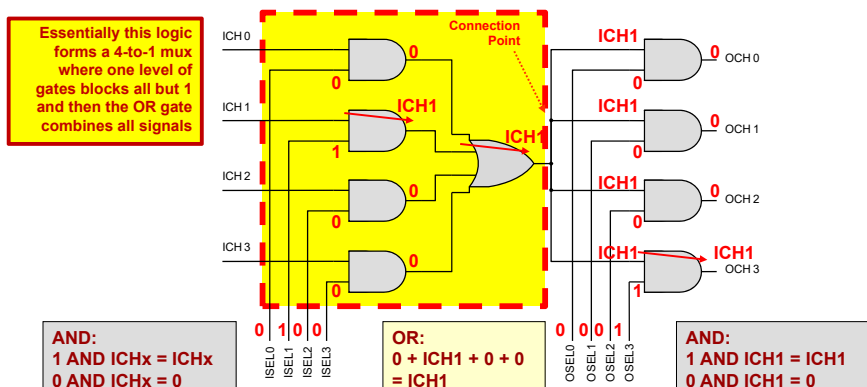- 1st Level of AND gates act as barriers only passing 1 channel
- OR gates combines 3 streams of 0's with the 1 channel that got passed (i.e. ICH1)
- 2nd Level of AND gates passes the channel to only the selected output



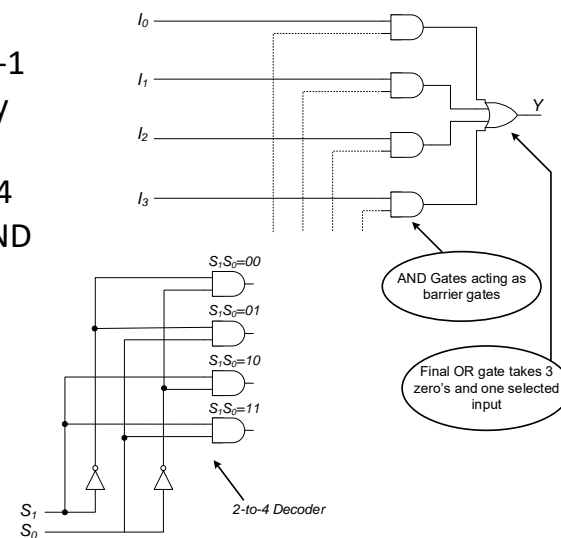
Exercise: Build a 4-to-1 mux

- Complete the 4-to-1 mux to the right by drawing wires between the 2-to-4 decode and the AND gates




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.




Building Wide Muxes

 - So far muxes only have single bit inputs...
 - I_0 is only 1-bit
 - I_1 is only 1-bit
- What if we still want to select between 2 inputs but now each input is a 4-bit number
- Use a 4-bit wide 2-to-1 mux




Building Wide Muxes

 - To build a 4-bit wide 2-to-1 mux, use 4 separate 2-to-1 muxes
- When $S=0$, all muxes pass their I_0 inputs which means all the A bits get through
- When $S=1$, all muxes pass their I_1 inputs which means all the B bits get through
- In general, to build an **m-bit wide n-to-1 mux**, use **m individual (separate) n-to-1 muxes**



Building Wide Muxes

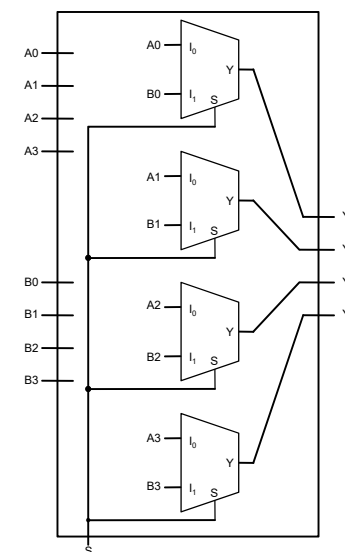
- To build a 4-bit wide 2-to-1 mux, use 4 separate 2-to-1 muxes
- When $S=0$, all muxes pass their I_0 inputs which means all the A bits get through
- When $S=1$, all muxes pass their I_1 inputs which means all the B bits get through
- In general, to build an **m-bit wide n-to-1 mux**, use **m individual (separate) n-to-1 muxes**



Exercise


- How many 1-bit wide muxes and of what size would you need to build a **4-to-1, 8-bit wide mux** (i.e. there are 4 numbers: $W[7:0]$, $X[7:0]$, $Y[7:0]$ and $Z[7:0]$ and you must select one)
- How many 1-bit wide muxes and of what size would you need to build a **8-to-1, 2-bit wide mux**?

Single-Cycle CPU

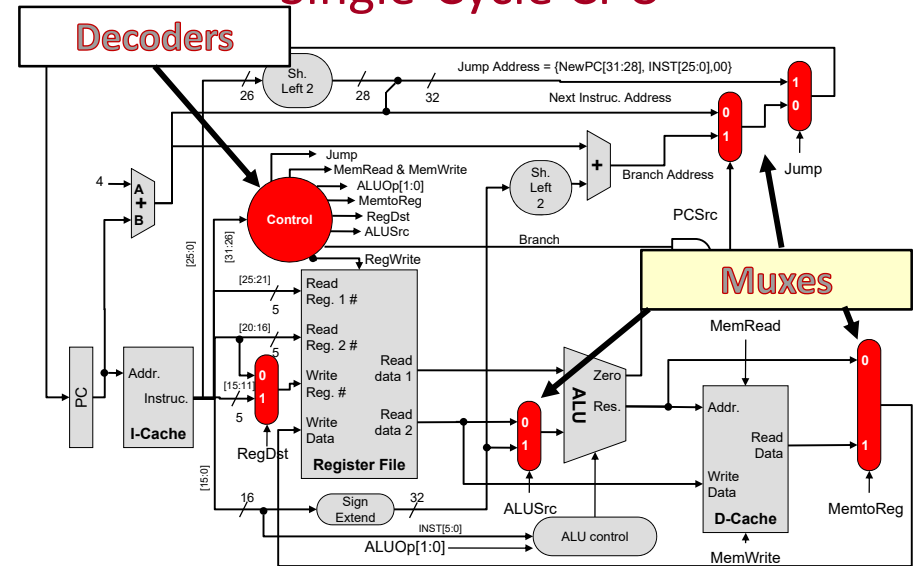


Building Large Muxes

 - Similar to a tournament of sports teams
 - Many teams enter and then are narrowed down to 1 winner
 - In each round winners play winners




Design an 8-to-1 mux with 2-to-1 Muxes

 

Cascading Muxes

- Use several small muxes to build large ones
- Rules
 1. Arrange the muxes in stages (based on necessary number of inputs in 1st stage)
 2. Outputs of 1 stage feed to inputs of the next
 3. All muxes in a stage connect to the same group of select bits
 - Usually, LSB connects to first stage
 - MSB connect to last stage

Building a 4-to-1 Mux

 


Building a 4-to-1 Mux

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Walk through an example:

$S_1 S_0 = 01$

 


Building a 4-to-1 Mux

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Walk through an example:

$S_1 S_0 = 01$

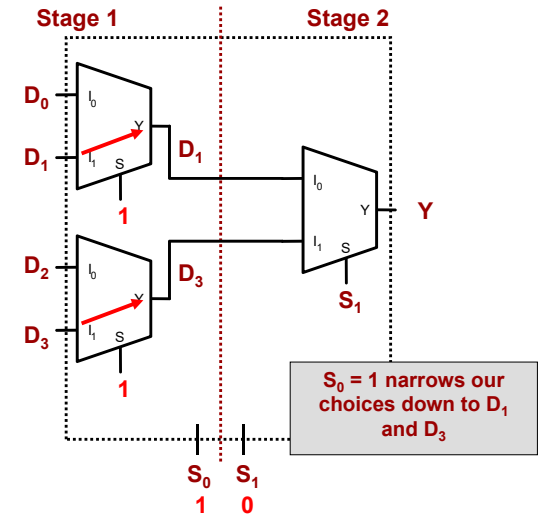


Building a 4-to-1 Mux

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Walk through an example:

S₁S₀ = 01

 

Exercise

- Create a 3-to-1 mux using 2-to-1 muxes
 - Inputs: I₀, I₁, I₂ and select bits S₁, S₀
 - Output: Y