

## Spiral 1 / Unit 3

Minterm and Maxterms

Canonical Sums and Products

2- and 3-Variable Boolean Algebra Theorems

DeMorgan's Theorem

Function Synthesis use Canonical Sums/Products

© Mark Redekopp

## Outcomes

- I know the difference between combinational and sequential logic and can name examples of each.
- I understand latency, throughput, and at least 1 technique to improve throughput
- I can identify when I need state vs. a purely combinational function
  - I can convert a simple word problem to a logic function (TT or canonical form) or state diagram
- I can use Karnaugh maps to synthesize combinational functions with several outputs
- I understand how a register with an enable functions & is built
- I can design a working state machine given a state diagram
- I can implement small logic functions with complex CMOS gates

## SYNTHESIZING LOGIC FUNCTIONS

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

1's Count of Inputs


I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## The Problem

- Given a logic function, how do we arrive at a circuit to implement this combinational function?
 
## Combining Functions


- Given intermediate functions F1 and F2, how could you use AND, OR, NOT to make G



X	Y	Z	F1	F2	G
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	0
 
## Combining Functions

- Given intermediate functions F1 and F2, how could you use AND, OR, NOT to make G



X	Y	Z	F1	F2	G
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	1	0	1
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	0




X	Y	Z	F1	F2	F1'	F2'	F1'F2'
0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	1
0	1	0	1	0	1	1	1
0	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1
1	0	1	1	0	1	1	1
1	1	0	1	0	1	1	1
1	1	1	1	1	1	0	0

$G = F1'F2'$
 
## Combining Functions


- Given intermediate functions F1 and F2, how could you use AND, OR, NOT to make H



X	Y	Z	F1	F2	H
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	0	0	1
 
## Question

- Is there a set of functions (F1, F2, etc.) that would allow you to build ANY 3-variable function  
– Think simple, think many



X	Y	Z	F1	F2	Fn	?
0	0	0				?
0	0	1				?
0	1	0				?
0	1	1				?
1	0	0				?
1	0	1				?
1	1	0				?
1	1	1				?



X	Y	Z	m0	m1	m2	m3	m4	m5	m6	m7	?
0	0	0	1	0	0	0	0	0	0	0	?
0	0	1	0	1	0	0	0	0	0	0	?
0	1	0	0	0	1	0	0	0	0	0	?
0	1	1	0	0	0	1	0	0	0	0	?
1	0	0	0	0	0	0	1	0	0	0	?
1	0	1	0	0	0	0	0	1	0	0	?
1	1	0	0	0	0	0	0	0	1	0	?
1	1	1	0	0	0	0	0	0	0	1	?

OR together any combination of m's

# Defining Minterms

- Remember these minterms are intermediate functions that we'll use to build larger functions
- Write the expression for each minterm of  $F(x,y,z)$

Row #	Minterm Expression	x	y	z	Minterms								
					$m_0$	$m_1$	$m_2$	$m_3$	$m_4$	$m_5$	$m_6$	$m_7$	
0	$m_0$	0	0	0	1	0	0	0	0	0	0	0	0
1	$m_1$	0	0	1	0	1	0	0	0	0	0	0	0
2	$m_2$	0	1	0	0	0	1	0	0	0	0	0	0
3	$m_3$	0	1	1	0	0	0	1	0	0	0	0	0
4	$m_4$	1	0	0	0	0	0	0	1	0	0	0	0
5	$m_5$	1	0	1	0	0	0	0	0	1	0	0	0
6	$m_6$	1	1	0	0	0	0	0	0	0	1	0	0
7	$m_7$	1	1	1	0	0	0	0	0	0	0	0	1

# Applying Minterms to Synthesize a Function

- Each numbered minterm checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the minterm will evaluate to 1 and thus the whole function will evaluate to 1.

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$P = m_2 + m_3 + m_5 + m_7$$

$$= x'yz' + x'yz + xy'z + xyz$$

when  $x,y,z = \{0,1,0\} = 2$  then

$$P = 0' \cdot 1 \cdot 0' + 0' \cdot 1 \cdot 0 + 0 \cdot 1' \cdot 0 + 0 \cdot 1 \cdot 0$$

$$= 1 + 0 + 0 + 0 = 1$$

when  $x,y,z = \{1,0,1\} = 5$  then

$$P = 1' \cdot 0 \cdot 1' + 1' \cdot 0 \cdot 1 + 1 \cdot 0' \cdot 1 + 1 \cdot 0 \cdot 1$$

$$= 0 + 0 + 1 + 0 = 1$$


when  $x,y,z = \{0,0,1\} = 1$  then

$$P = 0' \cdot 0 \cdot 1' + 0' \cdot 0 \cdot 1 + 0 \cdot 0' \cdot 1 + 0 \cdot 0 \cdot 1$$

$$= 0 + 0 + 0 + 0 = 0$$


# Checkers / Decoders

- The  $m_i$  functions on the previous slide are just AND gate checkers
  - That combination can be changed by adding inverters to the inputs
  - We can think of the AND gate as "checking" or "decoding" a specific combination and outputting a '1' when it matches.



X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

AND gate decoding (checking for) combination 101



X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

AND gate decoding (checking for) combination 000

# Minterms

- A minterm can be generated for every combination of inputs
- Each minterm is the AND'ing of variables that will evaluate to 1 for only that combination
- A minterm "checks" or "decodes" a specific input combination and outputs 1 when found

Minterm 3  
 $011 = x' \cdot y \cdot z = m_3$

Minterm 5  
 $101 = x \cdot y' \cdot z = m_5$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

To make the minterm, complement the variables that equal 0 and leave the variables in their true form that equal 1.

## Using Decoders to Implement Functions


- Given an any logic function, it can be implemented with the superposition of decoders/checkers

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	A
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	A	B
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders


X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

X	Y	Z	A	B	C
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	1

 
## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders



 
## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders



 
## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders


 
## Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders



# Minterm Definition

- Minterm:** A product term where each input variable of a function appears as exactly one literal

–  $f(x,y,z) =>$

- $x'y'z$  ✓
- $xyz$  ✓
- $x'y$  ✗
- $x+y+z$  ✗


# Minterms

- Consider  $F(A,B)$
- One minterm per combination of the input variables
- Only one minterm can evaluate to 1 at any time

A	B	F	$m_0$ $A'B'$	$m_1$ $A'B$	$m_2$ $A'B'$	$m_3$ $A \cdot B$
0	0	0	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	1

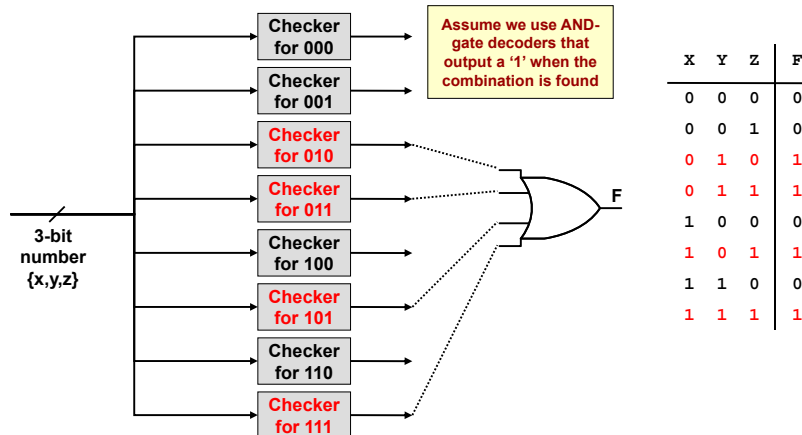
# Finding Equations/Circuits

- Given a function and checkers (called decoders) for each combination, we just need to OR together the checkers where  $F = 1$



 
# Control Signal Generation

- Other control signals are a function of the opcode
- We could write a full truth table or (because we are only implementing a small subset of instructions) simply decode the opcodes of the specific instructions we are implementing and use those intermediate signals to generate the actual control signals



 
Could generate each control signal by writing a full truth table of the 6-bit opcode



Simpler for human to design if we decode the opcode and then use individual "instruction" signals to generate desired control signals


# Control Signal Truth Table

OpCode [5:0]	R-Type	LW	SW	BEQ	J	Jump	Branch	Reg Dst	ALU Src	Memto-Reg	Reg Write	Mem Read	Mem Write	ALU Op[1]	ALU Op[0]
000000	1	0	0	0	0	0	0							1	0
100011	0	1	0	0	0	0	0							0	0
101011	0	0	1	0	0	0	0							0	0
000100	0	0	0	1	0	0	1							0	1
000010	0	0	0	0	1	1	0							X	X

 


# Control Signal Truth Table

OpCode [5:0]	R-Type	LW	SW	BEQ	J	Jump	Branch	Reg Dst	ALU Src	Memto-Reg	Reg Write	Mem Read	Mem Write	ALU Op[1]	ALU Op[0]
000000	1	0	0	0	0	0	0	1	0	0	1	0	0	1	0
100011	0	1	0	0	0	0	0	0	1	1	1	1	0	0	0
101011	0	0	1	0	0	0	0	X	1	X	0	0	1	0	0
000100	0	0	0	1	0	0	1	X	0	X	0	0	0	0	1
000010	0	0	0	0	1	1	0	X	X	X	0	0	0	X	X

 

# Control Signal Logic

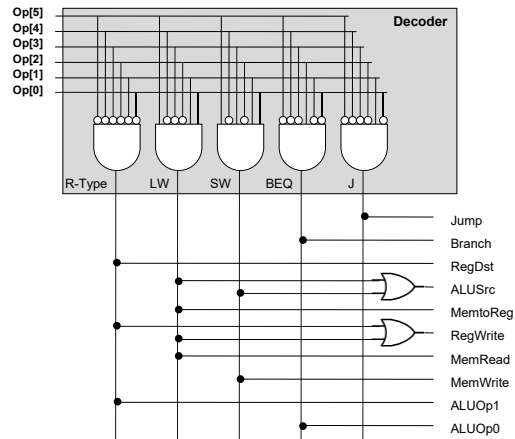


Using products of maxterms to implement a function

# MAXTERMS
 
## Question

- Is there a set of functions (F1, F2, etc.) that would allow you to build ANY 3-variable function
- Think simple, think many



X	Y	Z	F1	F2	Fn	?
0	0	0				?
0	0	1				?
0	1	0				?
0	1	1				?
1	0	0				?
1	0	1				?
1	1	0				?
1	1	1				?




X	Y	Z	m0	m1	m2	m3	m4	m5	m6	m7	?
0	0	0	1	0	0	0	0	0	0	0	?
0	0	1	0	1	0	0	0	0	0	0	?
0	1	0	0	0	1	0	0	0	0	0	?
0	1	1	0	0	0	1	0	0	0	0	?
1	0	0	0	0	0	0	1	0	0	0	?
1	0	1	0	0	0	0	0	1	0	0	?
1	1	0	0	0	0	0	0	0	1	0	?
1	1	1	0	0	0	0	0	0	0	1	?

OR together any combination of m<sub>i</sub>'s
 
## Question

- OR...this set of functions would also work.



X	Y	Z	M0	M1	M2	M3	M4	M5	M6	M7	?	G
0	0	0	0	1	1	1	1	1	1	1	?	1
0	0	1	1	0	1	1	1	1	1	1	?	0
0	1	0	1	1	0	1	1	1	1	1	?	1
0	1	1	1	1	1	0	1	1	1	1	?	0
1	0	0	1	1	1	1	0	1	1	1	?	1
1	0	1	1	1	1	1	1	0	1	1	?	1
1	1	0	1	1	1	1	1	1	0	1	?	0
1	1	1	1	1	1	1	1	1	1	0	?	1

AND together any combination of M<sub>i</sub>'s

G = M1 • M3 • M6

## Defining Maxterms

- Remember these maxterms are intermediate functions that we'll use to build larger functions
- Write the expression for each Maxterm of F(x,y,z)

Row #	Maxterm	x	y	z	Maxterms							
					M <sub>0</sub>	M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>	M <sub>4</sub>	M <sub>5</sub>	M <sub>6</sub>	M <sub>7</sub>
0	M <sub>0</sub>	0	0	0	0	1	1	1	1	1	1	1
1	M <sub>1</sub>	0	0	1	1	0	1	1	1	1	1	1
2	M <sub>2</sub>	0	1	0	1	1	0	1	1	1	1	1
3	M <sub>3</sub>	0	1	1	1	1	1	0	1	1	1	1
4	M <sub>4</sub>	1	0	0	1	1	1	1	0	1	1	1
5	M <sub>5</sub>	1	0	1	1	1	1	1	1	0	1	1
6	M <sub>6</sub>	1	1	0	1	1	1	1	1	1	0	1
7	M <sub>7</sub>	1	1	1	1	1	1	1	1	1	1	0

## Applying Maxterms to Synthesize a Function

- Each numbered maxterm checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the maxterm will evaluate to 0 and thus the whole function will evaluate to 0.

x	y	z	P	use...
0	0	0	0	M <sub>0</sub>
0	0	1	0	M <sub>1</sub>
0	1	0	1	
0	1	1	1	
1	0	0	0	M <sub>4</sub>
1	0	1	1	
1	1	0	0	M <sub>6</sub>
1	1	1	1	

$$P = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$= (x+y+z) \cdot (x+y+z') \cdot (x'+y+z) \cdot (x'+y'+z)$$

when x,y,z = {0,0,1} = 1 then

$$P = (0+0+1) \cdot (0+0+1') \cdot (0'+0+1) \cdot (0'+0'+1)$$

$$= 1 \cdot 0 \cdot 1 \cdot 1 = 0$$

when x,y,z = {1,1,0} = 6 then

$$P = (1+1+0) \cdot (1+1+0') \cdot (1'+1+0) \cdot (1'+1'+0)$$

$$= 1 \cdot 1 \cdot 1 \cdot 0 = 0$$

when x,y,z = {1,1,1} = 7 then

$$P = (1+1+1) \cdot (1+1+1') \cdot (1'+1+1) \cdot (1'+1'+1)$$

$$= 1 \cdot 1 \cdot 1 \cdot 1 = 1$$



# Maxterm Definition

- **Maxterm:** A sum term where each input variable of a function appears exactly once in that term (either in its true or complemented form)



–  $f(x,y,z) =>$

- $x'+y'+z$
- $x+y+z$
- $y+z'$
- $x'y'z'$



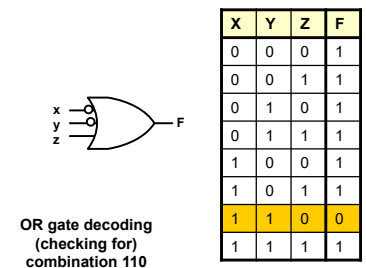 
# Checkers / Decoders

- An OR gate only outputs '0' for 1 combination
  - That combination can be changed by adding inverters to the inputs
  - We can think of the OR gate as “checking” or “decoding” a specific combination and outputting a '0' when it matches.


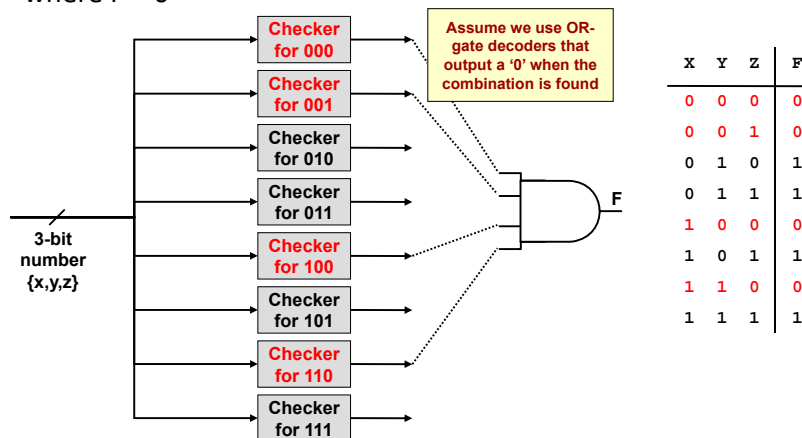
# Finding Equations/Circuits

- Given a function and checkers (called decoders) for each combination, we just need to AND together the checkers where  $F = 0$



# LOGIC FUNCTION NOTATION

## Canonical Sums

- We OR together all the minterms where  $F = 1$ 
  - ( $\Sigma$  = SUM or OR of all the minterms)

$$F = m_2 + m_3 + m_5 + m_7$$

Canonical Sum:

$$F = \sum_{xyz} (2, 3, 5, 7)$$

List the minterms where  $F$  is 1.

	X	Y	Z	F
$m_0$	0	0	0	0
$m_1$	0	0	1	0
$m_2$	0	1	0	1
$m_3$	0	1	1	1
$m_4$	1	0	0	0
$m_5$	1	0	1	1
$m_6$	1	1	0	0
$m_7$	1	1	1	1

## Canonical Products

- We AND together all the maxterms where  $F = 0$

$$F = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

Canonical Product:

$$F = \prod_{xyz} (0, 1, 4, 6)$$

List the maxterms where  $F$  is 0.

	X	Y	Z	F
$M_0$	0	0	0	0
$M_1$	0	0	1	0
$M_2$	0	1	0	1
$M_3$	0	1	1	1
$M_4$	1	0	0	0
$M_5$	1	0	1	1
$M_6$	1	1	0	0
$M_7$	1	1	1	1

## Canonical Form Practice

$$G = \sum_{XYZ} (\quad) = \prod_{XYZ} (\quad)$$

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


$$B = \sum_{X,Y,Z} (5,6,7)$$

$$F =$$

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1
 
## Logic Functions

- A logic function maps input combinations to an output value ('1' or '0')
- 3 possible representations of a function
  - Equation
  - Schematic
  - Truth Table
- Can convert between representations
- Truth table is only unique representation\*



\* Canonical Sums/Products (minterm/maxterm) representation provides a standard equation/schematic form that is unique per function

# Unique Representations

- Canonical => Same functions will have same representations
- Truth Tables along with Canonical Sums and Products specify a function *uniquely*
- Equations/circuit schematics are NOT inherently canonical

Truth Table

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Canonical Sum

$$P = \sum_{x,y,z} (2,3,5,7)$$

ON-Set of P (minterms)

Yields SOP equation, AND-OR circuit

Canonical Product


$$P = \prod_{x,y,z} (0,1,4,6)$$

OFF-Set of P (maxterms)

Yields POS equation, OR-AND circuit


 
# Example: Automobile Buzzer

- Consider an automobile warning Buzzer that sounds if you leave the Key in the ignition and the Door is open OR the Headlights are on and the Door is open.
- We can easily derive an equation and implementation:  $B = KD + HD$


  
# Example: Automobile Buzzer

- But we see that we can alter this equation...
  - From  $B = KD + HD$
  - To  $B = D(K+H)$ 
    - Buzzer sounds if the Door is open and *either* the Key is in the Ignition or the Headlights are on
- Which is better?
- What is the canonical minterm/maxterm representation?



# Example Form

- Given a function,  $B(D,K,H)$  we can define the minterm functions (which serve as intermediate functions) and then generate the overall function from the minterms
  - $B = \Sigma$
  - $B = \Pi$

Row	D	K	H	Minterm	Designation	Maxterm	Designation	B
0	0	0	0	$D' \cdot K' \cdot H'$	$m_0$	$D+K+H$	$M_0$	0
1	0	0	1	$D' \cdot K' \cdot H$	$m_1$	$D+K+H'$	$M_1$	0
2	0	1	0	$D' \cdot K \cdot H'$	$m_2$	$D+K'+H$	$M_2$	0
3	0	1	1	$D' \cdot K \cdot H$	$m_3$	$D+K'+H'$	$M_3$	0
4	1	0	0	$D \cdot K' \cdot H'$	$m_4$	$D'+K+H$	$M_4$	0
5	1	0	1	$D \cdot K' \cdot H$	$m_5$	$D'+K+H'$	$M_5$	1
6	1	1	0	$D \cdot K \cdot H'$	$m_6$	$D'+K'+H$	$M_6$	1
7	1	1	1	$D \cdot K \cdot H$	$m_7$	$D'+K'+H'$	$M_7$	1

## 2 & 3 Variable Theorems

<b>T6</b>	$X+Y = Y+X$	<b>T6'</b>	$X \cdot Y = Y \cdot X$	Commutativity
<b>T7</b>	$(X+Y)+Z = X+(Y+Z)$	<b>T7'</b>	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associativity
<b>T8</b>	$XY+XZ = X(Y+Z)$	<b>T8'</b>	$(X+Y)(X+Z) = X+YZ$	Distribution & Factoring
<b>T9</b>	$X + XY = X$	<b>T9'</b>	$X(X+Y) = X$	Covering
<b>T10</b>	$XY + XY' = X$	<b>T10'</b>	$(X+Y)(X+Y') = X$	Combining
<b>T11</b>	$XY + X'Z + YZ = XY + X'Z$	<b>T11'</b>	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$	Consensus
<b>DM</b>	$(X+Y)' = X' \cdot Y'$	<b>DM'</b>	$(X \cdot Y)' = X' + Y'$	DeMorgan's

## DeMorgan's Theorem

- Inverting output of an AND gate = inverting the inputs of an OR gate
- Inverting output of an OR gate = inverting the inputs of an AND gate

A function's inverse is equivalent to inverting all the inputs and changing AND to OR and vice versa

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

$\overline{A \cdot B}$



$\overline{A+B}$

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

$\overline{A+B}$




$\overline{A \cdot B}$

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0
 
## AND-OR / NAND-NAND


- Canonical Sums yield
  - AND-OR Implementation
  - NAND-NAND Implementation



||
 
## OR-AND / NOR-NOR



- Canonical Products yield
  - OR-AND Implementation
  - NOR-NOR Implementation



||

  
## Example: Automobile Buzzer

- Convert each implementation to use either just NOR or just NAND gates + inverters


 
## Convert to NAND-NAND

- Convert the 2-to-1 mux below to use just NAND or NOR gates?



## Logic Synthesis

- Describe the function
  - Usually with a truth table
- Find the sum of products or product of sums expression
  - Fewer 1's in the output => use canonical sum
  - Fewer 0's in the output => use canonical product
- Use Boolean Algebra (T8-T11) to find a simplified expression

## Exercise 1

- Synthesize this function in two ways
  - First use the canonical sum
  - Then use the canonical product

T8	$XY + XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

## Exercise 2

- Synthesize this function in two ways
  - First use the canonical sum
  - Then use the canonical product

<b>T8</b>	$XY + XZ = X(Y+Z)$	<b>T8'</b>	$(X+Y)(X+Z) = X+YZ$
<b>T9</b>	$X + XY = X$	<b>T9'</b>	$X(X+Y) = X$
<b>T10</b>	$XY + XY' = X$	<b>T10'</b>	$(X+Y)(X+Y') = X$
<b>T11</b>	$XY + X'Z + YZ = XY + X'Z$	<b>T11'</b>	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

I3	I2	I1	M1	M0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID (ie. 3, 2, or 1) that is ON (=1)

## Exercise 3

- Synthesize this function in two ways
  - First use the canonical sum
  - Then use the canonical product

<b>T8</b>	$XY + XZ = X(Y+Z)$	<b>T8'</b>	$(X+Y)(X+Z) = X+YZ$
<b>T9</b>	$X + XY = X$	<b>T9'</b>	$X(X+Y) = X$
<b>T10</b>	$XY + XY' = X$	<b>T10'</b>	$(X+Y)(X+Y') = X$
<b>T11</b>	$XY + X'Z + YZ = XY + X'Z$	<b>T11'</b>	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

1's Count of Inputs

I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1